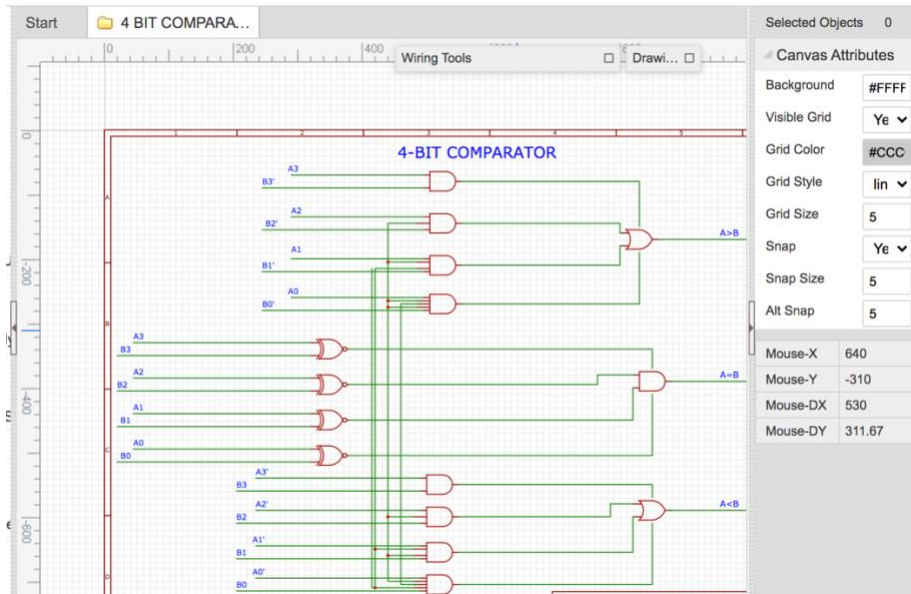


Yutong Wang 260839723  
Hongtao Xu 260773785

1. Briefly explain your VHDL code implementation of all circuits.


First of all, it is a 4-bit comparator with A and B inputs. I found the circuit of the 4-bit comparator and below is the truth table I found online:

**Table 1: Truth table for 4-bit**[illegible]

From the truth table we know that there are totally 8 inputs (4 for A and 4 for B) and 3 outputs in the right. The 3 cases labelled in the right -hand side:  $A=B$ ,  $A>B$  and  $A<B$ . While in this lab, we also need to think about the cases  $A\geq B$ ,  $A\leq B$  and overflow.


To be specific, A and B are assigned to 4 bits input respectively, they counted as <3 downto 0>. For the output: AgtBplusOne, AgteBplusOne, AltBplusOne, AlteBplusOne and AeqBplusOne. In this way, we can setup the testbench. The number of inputs for A and B are set into 16 loops respectively. A: for m in 0 to 15 loop; B: for n in 0 to 15 loop; a\_in <= std\_logic\_vector(to\_unsigned(m, 4)); b\_in <= std\_logic\_vector(to\_unsigned(n, 4));

Now is the design part. First of all, there are totally 5 cases: AgtBplusOne; AgteBplusOne; AltBplusOne; AlteBplusOne and AeqBplusOne. For the overflow= '1': B= '1111', if B+1, it would out of space for truth table. In this way, all of those cases call '0' which means overflow. Otherwise, if overflow is not happened (overflow = '0'), we compare the value A and B+1 and select the corresponding cases. For example, if  $A < B+1$  means that AltBplusOne = '1', otherwise AltBplusOne = '0'. Similar for all the other cases. In this way, we use the [if-then-else] statement check all the cases and get the corresponding statement. Finally, we could get the correct EPWave:

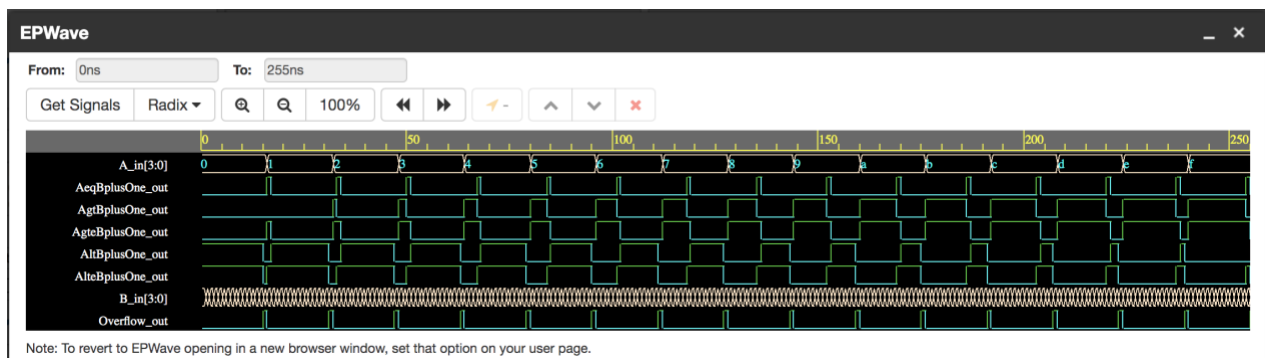


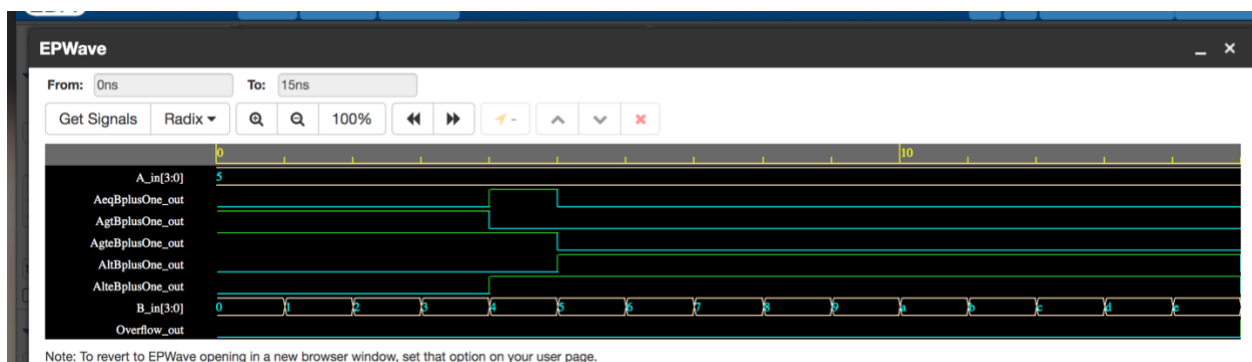2. Given that  $A = 510$ , provide a separate simulation plot that demonstrates all possible cases for the 4-bit comparator, including a separate plot for the case where overflow occurs. A total of four plots should be included. Explain each plot and mark all inputs and outputs clearly.


When  $A=5$  with base of 10, the overall EPWave:



 From this plot, we know that overflow would occur at  $B = '1110'$ , cause  $B+1$  then would out of the capacity.



 
That's the plot for  $A > B+1$  and  $A \geq B+1$ , for AgtBplusOne\_out = '1' happens when Bin = 0,1,10,11 in Binary (0,1,2,3 in Radix) and AgteBplusOne\_out = '1' happens when Bin = 0,1,10,11,100 in Binary (0,1,2,3,4 in Radix), which is one bit more than AgtBplusOne.




That's the plot for  $A < B+1$  and  $A \leq B+1$ . For AltBplusOne\_out = '1' happens since Bin = 5 (101) and AlteBplusOne\_out = '1' happens since Bin = 4, which is still one more number than AltBplusOne\_out. It is noticed that Bin=4 is commonly shared by both AlteBplusOne\_out and AgteBplusOne\_out.



 That's the plot for  $A = B+1$  happens when Bin = 4, is also commonly shared by both AlteBplusOne\_out and AgteBplusOne\_out.



 3. Perform timing analysis of the 4-bit comparator and find the critical path(s) of the circuit. What is the delay of the critical path(s)?



Optimized logic diagram for a 4-bit comparator

This is the optimized diagram of a 4-bit comparator I found online.

```
# Info: [670]: Finished synthesizing design.
# Info: [11019]: Total CPU time for synthesis: 0.6 s secs.
# Info: [11020]: Overall running time for synthesis: 0.6 s secs.
# Info: /home/runner/impl_1/precision_tech.sdc
# Info: [44856]: Total lines of RTL compiled: 58.
# Info: [44835]: Total CPU time for compilation: 0.0 secs.
# Info: [44513]: Overall running time for compilation: 1.0 secs.
# Info: [667]: Current working directory: /home/runner/impl_1.
# Info: [15333]: Doing rtl optimizations.
```

From the log on EDA playground I found that the running timing is 0.6s.

From the above circuit I found that the critical path is going through a NOR gate, then enter to a AND gate, enter to a OR gate and a NOT gate, finally going through a OR gate. The critical path would go through 5 gates.

From the above log screenshot we calculate delay of critical path =  $1s - 0.6s = 0.4s$

4. Report the number of pins and logic modules used to fit your 4-bit comparator design on the FPGA board.

The number of pins: used:14 and Avial 210.

The number of logic modules: used:9 and Avial:63400

Reference:

[http://users.encs.concordia.ca/~asim/COEN\\_6511/Projects/final6511report.pdf](http://users.encs.concordia.ca/~asim/COEN_6511/Projects/final6511report.pdf)

<https://easyeda.com/ankitjain21/4-bit-comparator>