

VHDL Assignment 3 Report

Yutong Wang 260839723

Hongtao Xu 260773785

1. Briefly explain your VHDL code implementation of all circuits.

- Half Adder: Use the truth table below we can obtain the relationship between inputs A, B and outputs S, C.

3.1.1 Half Adder

A(0)	B(0)	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

$S = A(0) \text{ XOR } B(0)$
 $C = A(0) \text{ AND } B(0)$

- Full Adder: First we draw the truth table of inputs (A, B, C_in) and outputs (C_out, S), then we use k-map to obtain the simplified SOP expression.

3.1.2 Full-Adder

C _{in}	A	B	C _{out}	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

C_{out}

A \ B	00	01	11	10
0	0	0	1	0
1	0	1	1	1

$C_{out} = AB + AC_{in} + BC_{in}$

S


A \ B	00	01	11	10
0	0	1	0	1
1	1	0	1	0

$S = A \oplus B \oplus C_{in}$

- Structural description of 4-bits RCA: The 4-bits RCA was divided into 4 stages as shown in the photo below. The first stage is a half adder and the

rest three stages are full adder.

 3.1.3 Structural Description of 4-bits RCA



Define signal $C(2 \text{ downto } 0)$ in `std_logic_vector`

- ↳ stage ① : Half adder
 $a \leftarrow A(0)$, $b \leftarrow B(0)$, $S \leftarrow S(0)$, $C \leftarrow C(0)$
- ↳ stage ② : Full Adder
 $a \leftarrow A(1)$, $b \leftarrow B(1)$, $S \leftarrow S(1)$,
 $C_in \leftarrow C(0)$, $C_out \leftarrow C(1)$
- ↳ stage ③ : Full Adder
 $a \leftarrow A(2)$, $b \leftarrow B(2)$, $S \leftarrow S(2)$,
 $C_in \leftarrow C(1)$, $C_out \leftarrow C(2)$
- ↳ stage ④ : Full Adder
 $a \leftarrow A(3)$, $b \leftarrow B(3)$, $S \leftarrow S(3)$,
 $C_in \leftarrow C(2)$, $C_out \leftarrow S(4)$

- Behavioral description of the 4-bits RCA: For the behavioral description, the arithmetic operator "+" was used. In order to use "+" operator, we must first define the two input signals `std_logic_vector` a and b to be unsigned vector. Secondly, because inputs A and B are 4 bits vectors and output S is 5 bits vectors, an extra bit of 0 is added in front of a and b so that they now have the same number of bits with s.
- Structural Description of a BCD Adder in VHDL: In a one bit BCD adder, the inputs signals are A(3 downto 0) and B(3 downto 0), the output signals are C and S(3 downto 0). Where C is the carry, $c=0$ when $(A+B)$ is less than or equal to 9, and $c=1$ when $(A+B)$ is greater than 9. Three intermediate signals were defined, (Z) represent the sum of A and B after the 4 bits RCA, (carry) represent the carry in the 4 bits RCA, (carry2) represents the carry in the 2 bits RCA. The circuit is shown below:

One digit BCD adder.

↳ Inputs: A, B : std_logic_vector (3 down to 0)


outputs: S : std_logic_vector (3 down to 0)

C : std_logic $\Rightarrow C$ is the Carry, used to check for overflow


$C = 0$ When $A+B \leq 9$

$C = 1$ When $A+B > 9$.

circuit diagram:

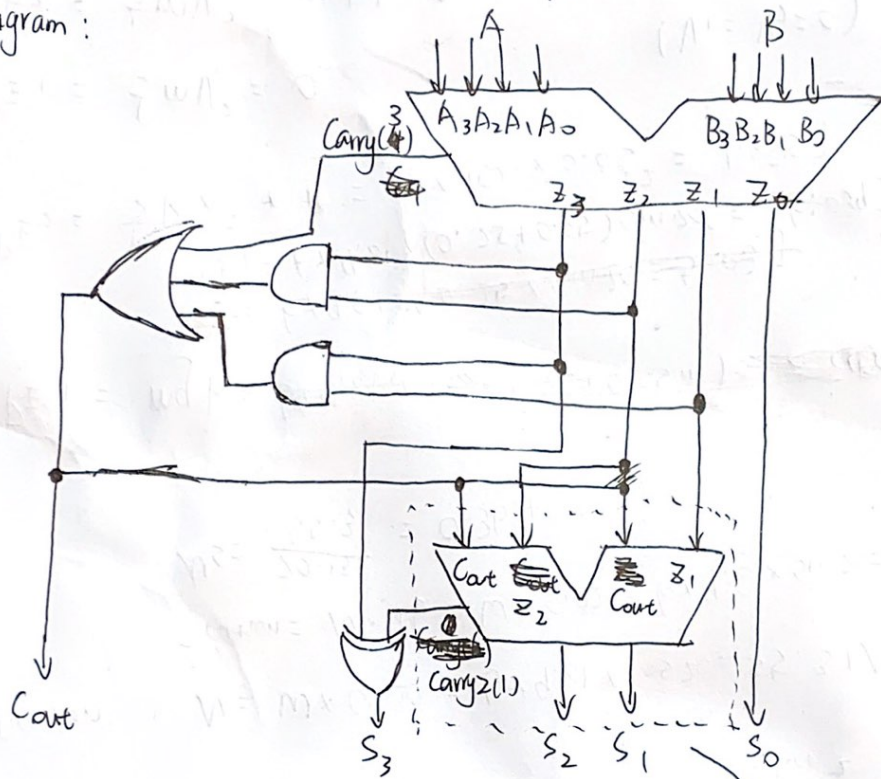


Where the 2-bits RCA is:

 


- Behavioral Description of a BCD Adder in VHDL : In the behavioral description, the input signals are A (3 downto 0), B (3 downto 0), and the output signals are S(3 downto 0) and C. Where c represent the carry, c=0 when (A+B) is less than or equal to 9, and c=1 when (A+B) is greater than 9. An intermediate signal z (4 downto 0) was defined, z represent the binary sum of (A+B), and since z has one more bits than A and B, so Z can handle the overflow. Another intermediate signal p (4 downto 0) was defined, where (P = Z+6), we use P instead of Z to represent (A+B) when (A+B) is greater than 9. Now in this case, the output s <= z(3 downto 0) when (c=0), else p(3 downto 0) when (c=1).

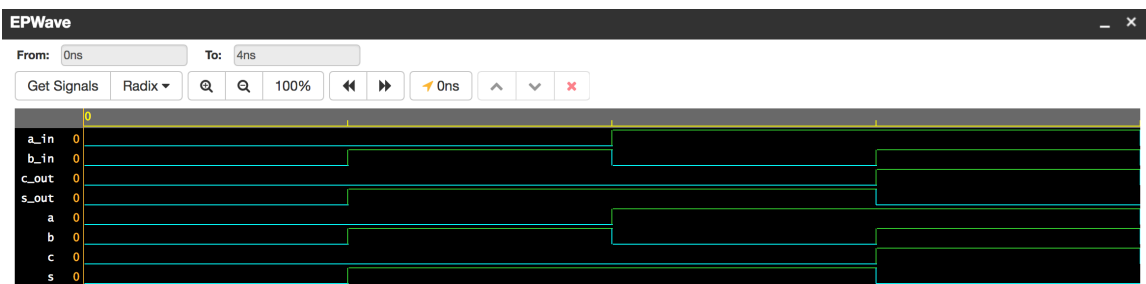2. Show representative simulation plots of the half-adder circuit for all possible input values.









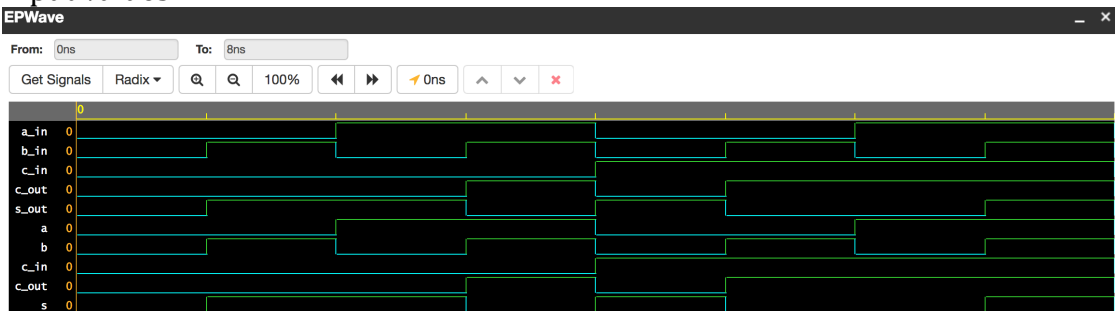
3. Show representative simulation plots of the full-adder circuit for all possible input values.



4. Show representative simulation plots of both behavioral and structural descriptions of the 4-bit RCA for all possible input values.

- For structural descriptions

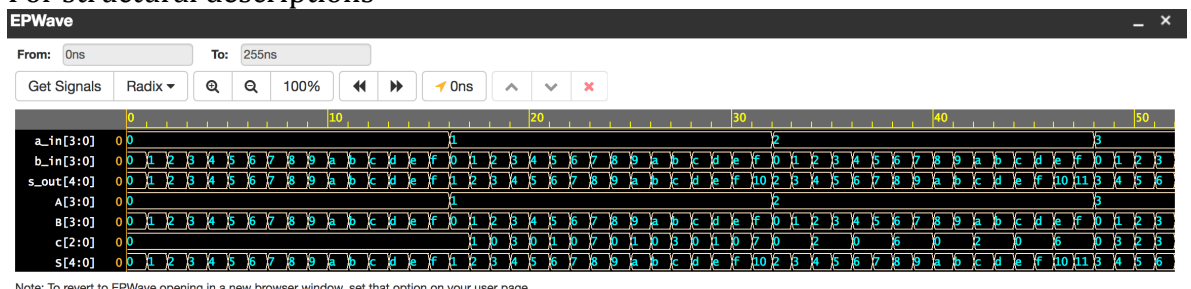

   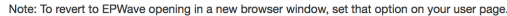 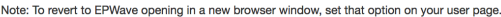

set_max_delay -from [get_ports A[*]] -to [get_ports S[*]] 20

set_max_delay -from [get_ports B[*]] -to [get_ports S[*]] 15

```

Log Share
Info: -- CTE report timing..
Info: CTE Path Report
Info: Critical path #1, (path slack = 15.000):, Logic Levels = 3
Info: SOURCE CLOCK: name: <not found> Path is min/max delay constrained
Info: NAME GATE DELAY ARRIVAL DIR FANOUT LEVEL
Info: A(3) (port) 0.000 dn
Info: A(3) (net) 0.000 1 0
Info: A_ibuf(3)/I IBUF 0.000 dn
Info: A_ibuf(3)/O IBUF 1.298 1.298 dn
Info: A_int(3) (net) 0.354 4 1
Info: ix47514z39522/I3 LUT5 1.652 dn
Info: ix47514z39522/O LUT5 0.124 1.776 up
Info: nx47514z1 (net) 0.333 1 2
Info: S_obuf(3)/I OBUF 2.109 up
Info: S_obuf(3)/O OBUF 2.891 5.000 up
Info: S(3) (net) 0.000 0 3
Info: S(3) (port) 5.000 up
Info: Minmax delay constraint: 20.000
Info: Source clock delay: - 0.000
Info: Dest clock delay: + 0.000
Info: Edge separation: 20.000
Info: Setup constraint: - 0.000
Info: Data required time: 20.000
Info: Data arrival time: - 5.000 ( 86.26% cell delay, 13.74% net delay )
Info: Slack: 15.000
Info: End CTE Analysis ..... CPU Time Used: 0 sec.

Info: -- CTE report timing..
Info: CTE Path Report
Info: Critical path #1, (path slack = 15.000):, Logic Levels = 3
Info: SOURCE CLOCK: name: <not found> Path is min/max delay constrained
Info: NAME GATE DELAY ARRIVAL DIR FANOUT LEVEL
Info: A(3) (port) 0.000 dn
Info: A(3) (net) 0.000 1 0
Info: A_ibuf(3)/I IBUF 0.000 dn
Info: A_ibuf(3)/O IBUF 1.298 1.298 dn
Info: A_int(3) (net) 0.354 4 1
Info: ix47514z39522/I3 LUT5 1.652 dn
Info: ix47514z39522/O LUT5 0.124 1.776 up
Info: nx47514z1 (net) 0.333 1 2
Info: S_obuf(3)/I OBUF 2.109 up
Info: S_obuf(3)/O OBUF 2.891 5.000 up
Info: S(3) (net) 0.000 0 3
Info: S(3) (port) 5.000 up
Info: Minmax delay constraint: 20.000
Info: Source clock delay: - 0.000
Info: Dest clock delay: + 0.000
Info: Edge separation: 20.000
Info: Setup constraint: - 0.000
Info: Data required time: 20.000
Info: Data arrival time: - 5.000 ( 86.26% cell delay, 13.74% net delay )
Info: Slack: 15.000
Info: End CTE Analysis ..... CPU Time Used: 0 sec.

```

7.

	RCA		One-digit BCD adder	
	Structural	Behavioral	Structural	Behavioral
Logic Utilization (in LUTs)	Used: 6 Avail: 63400	Used: 6 Avail: 63400	Used: 8 Avail: 63400	Used: 8 Avail: 63400
Total pins	Used: 13 Avail: 210	Used: 13 Avail: 210	Used: 13 Avail: 210	Used: 13 Avail: 210